

Transient Phenomena course (MPA-PRJ)

Assignment 1

Enter your BUT ID here, each digit in a separate cell.

ID:

2	8	5	2	6	9
---	---	---	---	---	---

The individual assignment is then generated in the sheet "Assignment1".

Instructions:

The assignment should be either hand-written or done on computer, but you cannot combine these two! If combined, the grade is automatically zero.

If the assignment is hand-written, use only the blank sheets (no lines) and your writing has to be legible.

Always put formula first, then substitute the numerical values and give the result with corresponding unit.

You must draw equivalent impedance diagrams and indicate their simplification to the resulting impedance.

Calculation is done according to the current version of IEC 60909-0 standard. Correction factors are considered except for three-winding transformer.

Calculation is done in per unit system with a given base.

You must give the conclusion to the assignment.

The assignment solution has to be compiled as one pdf file and submitted via the elearning.

Submission deadline is mandatory and cannot be extended.


Teachers will answer only specific questions, they will not provide a step-by-step guide!

Teachers will not check your assignment before its submission.

ASSIGNMENT 1

Calculate the initial short circuit currents in kA in bus number ### in the given network. Use only reactances. Correction factors are considered, except for 3-winding transformer. Voltage factor $c = 1.1$.

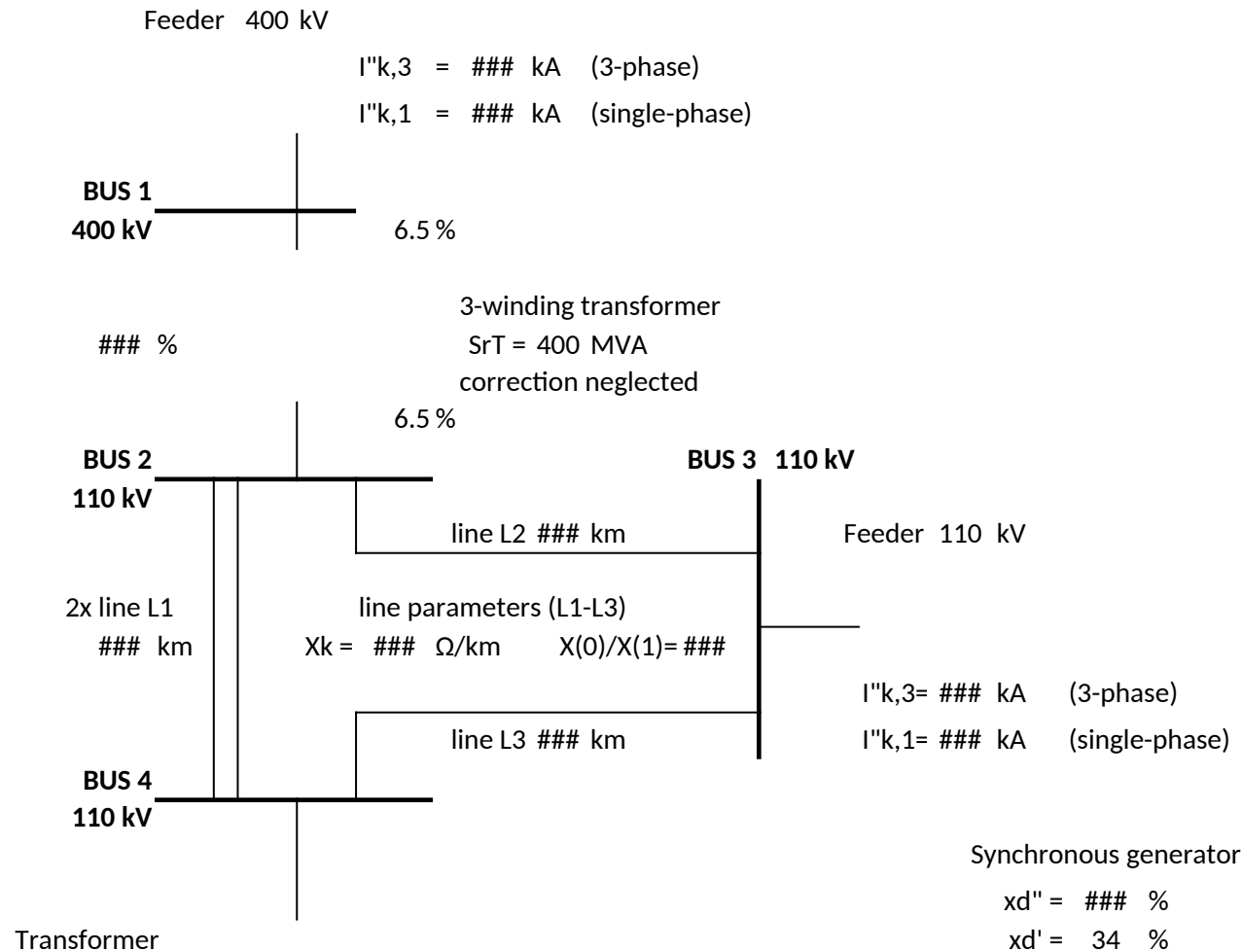Calculation should be performed in per unit values with a base power of ### MVA.



SrT = 65 MVA


ek% = 11.5 %

xd = ### %

VrG = 10 kV

PrG = 55 MW

cos φ rG = 0.85

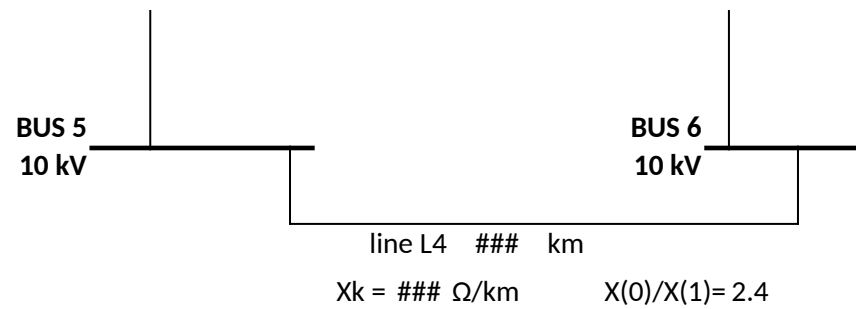

Assignment 1 – Solution

Bus 3 (110 kV) | Sbase = 100 MVA | c = 1.1

Element	Parameter	Value	Unit	Note
Task	Bus number to calculate	3		
Base	Base power Sbase	100	MVA	
Base	Voltage base (Bus 1)	400	kV	
Base	Voltage base (Bus 2,3,4)	110	kV	
Base	Voltage base (Bus 5,6)	10	kV	
Base	Zbase at 400 kV	1600	Ω	
Base	Zbase at 110 kV	121	Ω	
Base	Zbase at 10 kV	1.0	Ω	
Feeder Q1	Voltage	400	kV	
Feeder Q1	I"k,3	18	kA	
Feeder Q1	I"k,1	14.5	kA	
3WT	Rated power SrT	400	MVA	

3WT	ukHM (H-winding to M-winding)	12.0	%
3WT	ukHT (H-winding to T-winding)	6.5	%
3WT	ukMT (M-winding to T-winding)	6.5	%
2×L1	Length (each line)	98	km
L1–L3	Positive-seq reactance X_k	0.31	Ω/km
L1–L3	Zero-seq ratio X_0/X_1	3.3	—
L2	Length	70	km
L3	Length	117	km
Feeder Q2	Voltage (at Bus 3)	110	kV
Feeder Q2	$I''_{k,3}$	11.8	kA
Feeder Q2	$I''_{k,1}$	7.9	kA
Transformer T2	Rated power S_{rT}	65	MVA
Transformer T2	$e_k\%$	11.5	%
Generator G	x''_d (subtransient)	15.0	%
Generator G	x'_d (transient)	34	%
Generator G	x_d (synchronous)	129	%
Generator G	V_rG (rated voltage)	10	kV

Generator G	PrG (rated power)	55	MW
Generator G	cos φrG	0.85	—
Line L4	Length	14	km
Line L4	Xk	0.26	Ω/km
Line L4	X0/X1	2.4	—

2. PER-UNIT CONVERSIONS OF NETWORK ELEMENTS

Element	Formula	Result (pu)	Description
Feeder Q1 (400 kV)			
Z1_Q1	$c \cdot V_n / (\sqrt{3} \cdot I''_{k,3}) = 1.1 \times 400 / (\sqrt{3} \times 18)$	14.113 Ω → 0.00882 pu	pos. seq.
Z0_Q1	$\sqrt{3} \cdot c \cdot V_n / I''_{k,1} - 2 \cdot Z_1 = \sqrt{3} \times 1.1 \times 400 / 14.5 - 2 \times 14.113$	24.333 Ω → 0.01521 pu	zero seq.

3-Winding Transformer (correction neglected)

ukH	$(uk_{HM} + uk_{HT} - uk_{MT})/2 = (12 + 6.5 - 6.5)/2$	6.0%	ukH
-----	--	-------------	-----

ukM	$(uk_{HM} + uk_{MT} - uk_{HT})/2 = (12 + 6.5 - 6.5)/2$	6.0%	ukM
ukT	$(uk_{HT} + uk_{MT} - uk_{HM})/2 = (6.5 + 6.5 - 12)/2$	0.5%	ukT
xH	$uk_H\% \times S_{base}/S_{rT} = 0.06 \times 100/400$	0.01500 pu	xH [pu]
xM	$uk_M\% \times S_{base}/S_{rT} = 0.06 \times 100/400$	0.01500 pu	xM [pu]
xT	$uk_T\% \times S_{base}/S_{rT} = 0.005 \times 100/400$	0.00125 pu	xT [pu]

Lines (Xk = 0.31 Ω/km, X0/X1 = 3.3, Zbase = 121 Ω)

x1_2L1	$0.31 \times 98 / (2 \times 121)$	0.12554 pu	pos. seq.
x0_2L1	$3.3 \times 0.31 \times 98 / (2 \times 121)$	0.41427 pu	zero seq.
x1_L2	$0.31 \times 70 / 121$	0.17934 pu	pos. seq.
x0_L2	$3.3 \times 0.31 \times 70 / 121$	0.59182 pu	zero seq.
x1_L3	$0.31 \times 117 / 121$	0.29975 pu	pos. seq.
x0_L3	$3.3 \times 0.31 \times 117 / 121$	0.98918 pu	zero seq.
x1_L2 L3	$x1_{L2} \cdot x1_{L3} / (x1_{L2} + x1_{L3})$	0.11221 pu	pos. seq.
x0_L2 L3	$x0_{L2} \cdot x0_{L3} / (x0_{L2} + x0_{L3})$	0.37028 pu	zero seq.

Feeder Q2 (110 kV)

Z1_Q2	$c \cdot V_n / (\sqrt{3} \cdot I''_{k,3}) = 1.1 \times 110 / (\sqrt{3} \times 11.8)$	5.920 Ω → 0.04893 pu	pos. seq.
-------	--	-----------------------------	-----------

Z0_Q2

$$\sqrt{3} \cdot c \cdot V_n / I''_{k,1} - 2 \cdot Z_1 =$$
$$\sqrt{3} \times 1.1 \times 110 / 7.9 - 2 \times 5.920$$

14.688 Ω →

0.12139 pu

zero seq.

Transformer T2 (YNd assumed)

xT2

$$e_k \% \times S_{base} / S_{rT} =$$
$$0.115 \times 100 / 65$$

0.17692 pu

Synchronous Generator

SrG

$$PrG / \cos \varphi_{rG} = 55 / 0.85$$

64.706 MVA

sinϕrG

$$\sqrt{(1 - 0.85^2)}$$

0.52678

x''d (sys)	$x''d \times S_{base}/S_{rG} = 0.15 \times 100/64.706$	0.23182 pu	system base
KG	$c/(1+x''d \times \sin \phi_{rG}) = 1.1/(1+0.15 \times 0.52678)$	1.01945	correction factor
x''dK	$KG \times x''d_{sys} = 1.01945 \times 0.23182$	0.23633 pu	corrected x''d
Line L4			
x1_L4	$0.26 \times 14/1.0$	3.6400 pu	pos. seq.
x0_L4	$2.4 \times 0.26 \times 14/1.0$	8.7360 pu	zero seq.
Zgen_Bus4	$x''dK + x1_{L4} + xT2 = 0.23633 + 3.64 + 0.17692$	4.0532 pu	gen. branch at Bus 4

ZT2_Bus4(0) xT2 = 0.17692 **0.17692 pu** zero seq. shunt

3. EQUIVALENT CIRCUIT REDUCTION — Node Admittance Method

Network topology: Q1 → Bus1 → [xH] → S → [xM] → Bus2 → [2×L1] → Bus4 → [L2||L3] → Bus3 (fault bus)

Q2 → Bus3 (direct) | Generator → L4 → T2 → Bus4 | S → [xT] → Bus3 (direct T-winding)

Star-point S replaces 3WT. Bus 1 folded as shunt at S: $y_S = 1/(z1_Q1 + xH)$. T2 and generator folded as shunt at Bus 4.

Positive-Sequence Admittance Matrix Y1 (nodes: S, Bus2, Bus3, Bus4)

	S	Bus 2	Bus 3	Bus 4	Diagonal composition
S	908.647	-66.667	-800.000	0.000	$1/(z1_Q1+xH) + 1/xM + 1/xT$
Bus 2	-66.667	74.632	0.000	-7.966	$1/xM + 1/x1_2L1$

Bus 3					$\frac{1}{x_T} + \frac{1}{z1_Q2} + \frac{1}{x1_L2} L3$
	-800.000	0.000	829.350	-8.912	

Bus 4					$\frac{1}{x1_2L1} + \frac{1}{x1_L2} L3 + \frac{1}{Zgen_Bus4}$
	0.000	-7.966	-8.912	17.125	

$Z1, Bus3 = [Y1^{-1}]_{33} = 0.016510 \text{ pu}$

Zero-Sequence Admittance Matrix Y0 (nodes: S, Bus2, Bus3, Bus4)

3WT grounding: YNynyn — T2: YNd (delta on LV side blocks zero-seq from generator)

	S	Bus 2	Bus 3	Bus 4	Diagonal composition
S	899.771	-66.667	-800.000	0.000	$\frac{1}{(z0_Q1+xH)} + \frac{1}{xM} + \frac{1}{x_T}$
Bus 2	-66.667	69.081	0.000	-2.414	$\frac{1}{xM} + \frac{1}{x0_2L1}$
Bus 3	-800.000	0.000	810.938	-2.701	$\frac{1}{x_T} + \frac{1}{z0_Q2} + \frac{1}{x0_L2} L3$

Bus 4					$\frac{1}{x_{0_2L1} + 1/x_{0_L2} L3 + 1/x_{T2}}$
	0.000	-2.414	-2.701	10.767	

$$Z_{0, Bus3} = [Y_0^{-1}]_{33} = 0.023479 \text{ pu}$$

4. INITIAL SHORT-CIRCUIT CURRENT CALCULATION AT BUS 3 (110 kV)

$$I_{base} = S_{base} / (\sqrt{3} \cdot V_{base}) = 100 / (\sqrt{3} \times 110) = 0.52486 \text{ kA}$$

3-Phase Symmetrical Short-Circuit Current $I''_{k,3}$

Formula: $I''_{k,3} = c \cdot I_{base} / Z_{1_Bus3}$

Substitution: $I''_{k,3} = 1.1 \times 0.52486 / 0.016510$

RESULT: $I''_{k,3} = 34.97 \text{ kA (3-phase)}$

Single-Phase-to-Earth Short-Circuit Current $I''_{k,1}$

Formula: $I''_{k,1} = \sqrt{3} \cdot c \cdot I_{base} / (2 \cdot Z_{1_Bus3} + Z_{0_Bus3})$

Substitution: $I''_{k,1} = \sqrt{3} \times 1.1 \times 0.52486 / (2 \times 0.016510 + 0.023479)$

$$= 1.0000 / (0.033020 + 0.023479) = 1.0000 / 0.056499$$

RESULT: $I''_{k,1} = 17.70 \text{ kA (single-phase-to-earth)}$

5. SUMMARY

Quantity	Value	Unit	Comment
Z1_Bus3 (Thevenin positive-seq)	0.01651	pu	Obtained from $[Y1^{-1}]_{33}$
Z0_Bus3 (Thevenin zero-seq)	0.02348	pu	Obtained from $[Y0^{-1}]_{33}$
Ibase at 110 kV	0.52490	kA	$S_{base}/(\sqrt{3} \cdot V_{base})$
I"k,3 (3-phase fault at Bus 3)	34.97000	kA	$c \cdot I_{base}/Z1$
I"k,1 (1-phase fault at Bus 3)	17.70000	kA	$\sqrt{3} \cdot c \cdot I_{base}/(2Z1+Z0)$

6. CONCLUSION

The initial short-circuit currents at Bus 3 (110 kV) are:

$I''_{k,3} = 34.97 \text{ kA}$ (3-phase)

$I''_{k,1} = 17.70 \text{ kA}$ (single-phase-to-earth)

The 3-phase fault current is mainly fed through the 3-winding transformer from the 400 kV feeder. The generator's contribution is small because of the high impedance of line L4 at the 10 kV level. The single-phase current is lower than the 3-phase value, which is consistent with $Z_0 > Z_1$.